

Code : 100306

**B. Tech 3rd Semester Exam., 2019
(New Course)**

ELECTRICAL CIRCUIT ANALYSIS

Time : 3 hours

Full Marks : 70

Instructions :

- (i) The marks are indicated in the right-hand margin.
- (ii) There are **NINE** questions in this paper.
- (iii) Attempt **FIVE** questions in all.
- (iv) Question No. 1 is compulsory.

1. Answer any seven of the following as directed : 2×7=14

- (a) Using the superposition theorem, determine the current through resistor R_2 for the network shown in Fig. 1 :

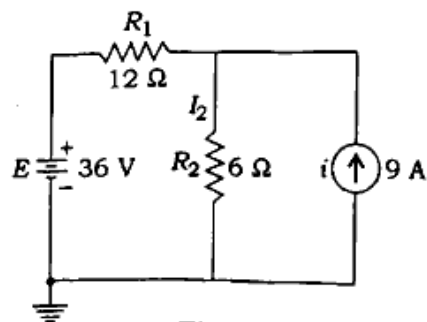


Fig. 1

20AK/303

(Turn Over)

(2)

- (b) Demonstrate why superposition theorem is not used for power calculation. Take Fig. 1 to justify your answer.
- (c) A passive network in the s-domain is shown in Fig. 2 :

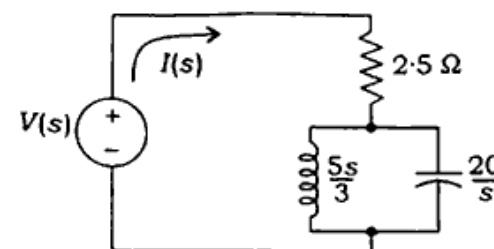


Fig. 2

Obtain the network function for the current $I(s)$ due to an input voltage $V(s)$.

- (d) Find the Thévenin equivalent circuit for the network in the shaded area of the Fig. 3 shown below :

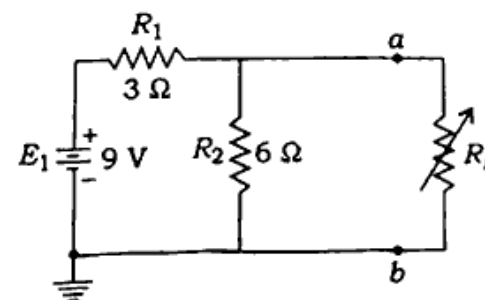


Fig. 3

20AK/303

(Continued)

- (e) Find the Norton equivalent circuit for the network external to the $9\ \Omega$ resistor shown in Fig. 4 :

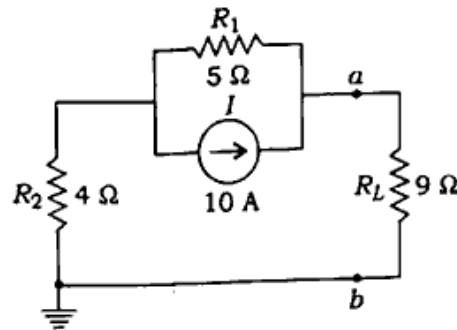


Fig. 4

- (f) Show that $AD - BC = 1$.
- (g) A network with 5 independent loops and 7 nodes will have ____ number of branches in the electrical network.
(Fill in the blank)

- (h) The time-constant of the circuit shown in Fig. 5 is RC sec

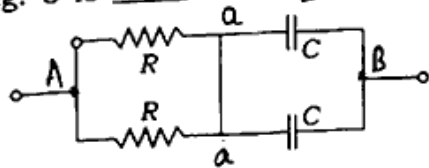


Fig. 5

(Fill in the blank)

(Turn Over)

- (i) In the circuit shown in Fig. 6, the initial voltage across the capacitor is 4 V. Switch S_1 is closed at $t = 0$. The charge (in μC) lost by the capacitor from $t = 25\ \mu\text{s}$ to $t = 100\ \mu\text{s}$ is ____.

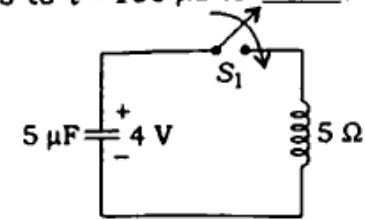


Fig. 6

(Fill in the blank)

- (ii) The Z -matrix of a two-port network is given as

$$Z = \begin{bmatrix} 0.9 & 0.2 \\ 0.2 & 0.6 \end{bmatrix}$$

Find the parameters Y_{21} and Y_{22} .

- (a) Find the Thévenin circuit for the network within the shaded area of Fig. 7 shown below :

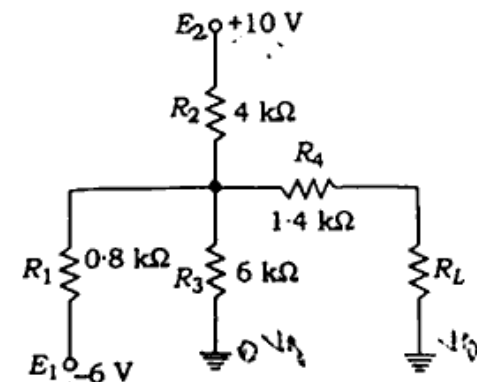


Fig. 7



State maximum power transfer theorem. Prove that efficiency of the circuit under maximum power transfer condition is 50%.

2+5

3. (a) A voltage $v = 140\cos(\omega t)$ is connected across an impedance $Z = 5\angle -60^\circ$. The voltage v results in a current $i = 28\cos(\omega t + 60^\circ)$. Calculate the power $p(t)$.

3

- (b) Define complex power, apparent power and power triangle.

3

- (c) Define half-power frequency. Find the condition of resonance in a parallel R - L - C circuit.

1+3

- (d) For the series R - L - C circuit show in Fig. 8, find the resonant frequency $\omega_0 = 2\pi f_0$:

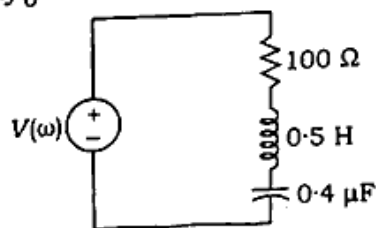


Fig. 8

Also obtain the half-power frequencies and the bandwidth.

4

(Turn Over)



- (a) State reciprocity theorem. Verify the reciprocity theorem for the circuit shown in Fig. 9 :

2+5

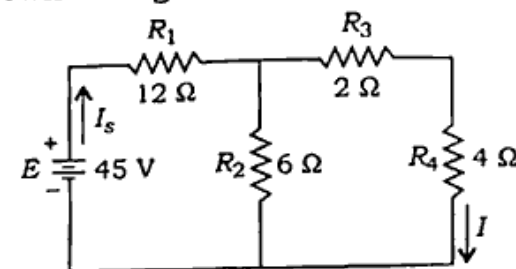


Fig. 9

- (b) The analysis of a transistor network resulted in the reduced equivalent in Fig. 10 shown below :

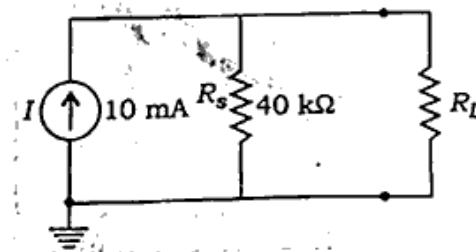


Fig. 10

Find the load resistance that will result in maximum power transfer to the load, and also find the maximum power delivered.

5

- (c). Define supermesh and supernode.

2

5. (a) Derive an expression of r.m.s. value of a half-wave rectified voltage output.

3

- (b) $E = 150 \sin(314t)$ is applied to a device which offers a resistance of 20Ω to the flow of current in one direction while preventing the flow of current in opposite direction. Calculate the r.m.s., average value and form factor for the current over one cycle.

7

- (c) A coil takes a current of 2 A when connected to 240 V, 50 Hz sinusoidal supply and consumes 200 watt power. Calculate the resistance, inductance and impedance of the coil.

4

6. (a) A circuit consists of series combination of resistance of 6Ω , inductance of 0.4 H , and a variable capacitor across 100 V, 50 Hz supply. Calculate the (i) value of capacitor at resonance, (ii) voltage drop across capacitor and (iii) Q-factor of the coil.

6

- (b) Find the Laplace transform of $f(t) = 1 - e^{-at}$, where a is a constant.

3

- (c) Find inverse Laplace of

$$F(s) = \frac{(s+1)}{s(s^2 + 4s + 4)}$$

5

7. (a) In the series $R-L-C$ circuit shown in Fig. 11, there is no initial charge on the capacitor :

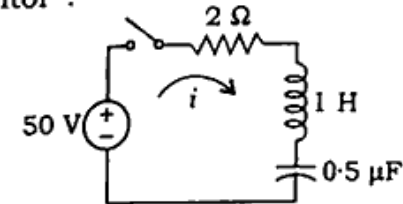


Fig. 11

If the switch is closed at $t = 0$, determine the resulting current.


5

- (b) Define transfer function. What are the significances of poles and zeroes? 2+2
- (c) Derive the impulse response of series $R-L$ circuit. 4
- (d) Draw the phasor diagram of an ideal transformer. 1



- (a) Define transmission parameter. Find the condition of reciprocity of h -parameters. 1+3

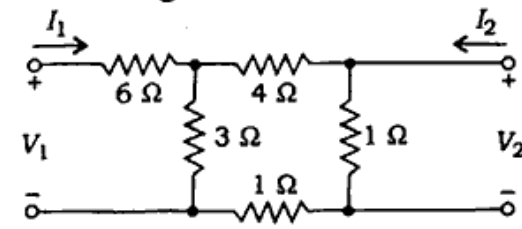- (b) Find the Z -parameters of the circuit shown in Fig. 12 : 5



(All resistances are in ohm)

Fig. 12

- (c) Two two-port networks a and b , with open-circuit impedances Z_a and Z_b , are connected in series. Derive the Z -parameters equations. 5

9. (a) Find the incidence matrix of the network shown in Fig. 13 : 5

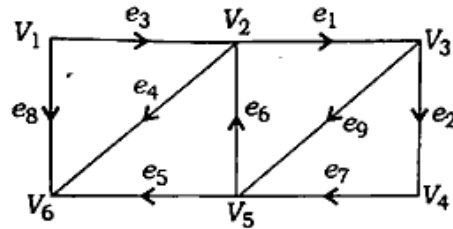


Fig. 13

- (b) Find out the cut-set matrix of the network shown in Fig. 14 : 5

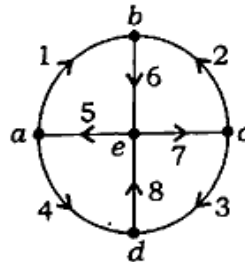


Fig. 14

- (c) Show that the steady-state errors of a first-order system with ramp input is equal to its time constant (T). 4
