

**B.Tech 3rd Semester Exam., 2019
(New Course)**

NETWORK THEORY

Time : 3 hours

Full Marks : 70

Instructions :

- (i) The marks are indicated in the right-hand margin.
- (ii) There are **EIGHT** questions in this paper.
- (iii) Attempt **FIVE** questions in all.
- (iv) Question No. 1 is compulsory.

1. Answer the following questions in brief
(any seven) : 2×7=14

- (a) Define the term complex frequency.
- (b) Write Z parameters in terms of ABCD parameters.
- (c) Define twig and link.
- (d) What do you mean by transfer function?
- (e) How can you say that a network is stable? Give definition.

(f) Write down all the properties of loop impedance matrix.

(g) Explain the following terms with reference to network topology :

- (i) Tree
- (ii) Twig and link
- (iii) Incidence matrix
- (iv) Oriented graph

(h) Write the Laplace transform of—

- (i) unit step;
- (ii) unit impulse;
- (iii) unit ramp.

(i) Explain the following terms with the help of examples :

- (i) Causal and Non-causal systems
- (ii) Time variant and time invariant systems
- (iii) Continuous and discrete-time signals
- (iv) Deterministic and probabilistic signals

http://www.akubihar.com

http://www.akubihar.com

http://www.akubihar.com

http://www.akubihar.com

2. (a) For the given reduced incidence matrix, draw the graph and hence obtain the f -cut set matrix : 6


$$\begin{bmatrix} 0 & 0 & 1 & 1 & 1 & 0 & -1 \\ 0 & 1 & 0 & 0 & -1 & 1 & 1 \\ -1 & 0 & 1 & 0 & 0 & -1 & 0 \end{bmatrix}$$

- (b) State and prove convolution theorem for Laplace transform. 8

3. (a) In a linear two-port network, $V_1(t)$ and $V_2(t)$ be the input voltage and its response at the output, $V_2(t) = te^{-2t}u(t)$. If the response to an impulse voltage be given by $V(t) = (e^{-t} + e^{-2t})u(t)$. Find the $V_1(t)$ as well as the transfer function of the network. 8

- (b) Explain in detail band stop filter, with proof. 8

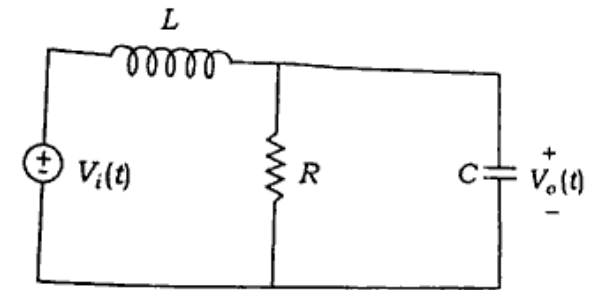4. (a) Determine what type of filter is shown in figure below. Calculate the corner or cut-off frequency. Take, $R = 2 \text{ k}\Omega$, $L = 2 \text{ H}$, and $C = 2 \mu\text{F}$: 8




- (b) Explain the parallel R - L - C resonance. Give essential equations and waveforms. 6

5. (a) Design a constant k low-pass filter having cut-off frequency 2.5 kHz and design resistance $R_0 = 700 \Omega$. Also, find the frequency at which this filter produces the attenuation of 19.1 dB . Find its characteristic impedances and phase constants at pass band and stop or attenuation band. 8

(5)

(b) What do you mean by 'POLES' and 'ZEROS' of a given network transfer function? What are the significances and limitations of network transfer function? Explain the complex frequency in the circuit theory. 6

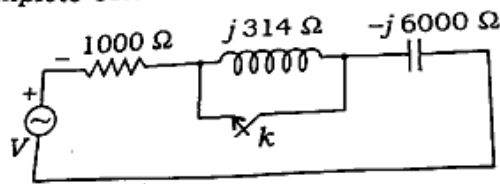6. In the following figure with switch open, steady state is reached with $v = 100 \sin 314 t$ volts. The switch is closed at $t = 0$. The circuit is allowed to come to steady state again. Determine the steady-state current and complete solution of transient current : 14



7. A network has two input terminals a, b and output terminals c, d . The input impedance with $c-d$ open circuited is $(250 + j100) \Omega$ and with $c-d$ short circuited is $(400 + j3000) \Omega$. The impedance across $c-d$ with $a-b$ open circuited is 200Ω . Determine the equivalent, T network parameters. 14

(6)

8. (a) What do you mean by 'Positive Real Function'? What are the properties associated with PRF? What are the significances of PRF? 7

(b) What are the properties of Hurwitz polynomial? Test whether the polynomial is Hurwitz or not.

$$F(s) = s^7 + 2s^6 + 2s^5 + s^4 + 4s^3 + 8s^2 + 8s + 4 \quad 7$$

http://www.akubihar.com
 Whatsapp @ 9300930012
 Your old paper & get 10/-
 पुराने पेपर्स भिजे और 10 रुपये पायें,
 Paytm or Google Pay से