

## B.Tech 6th Semester Exam., 2016

## INTELLIGENT INSTRUMENTS

Time : 3 hours

akubihar.com

Full Marks : 70

Instructions :

- (i) The marks are indicated in the right-hand margin.
- (ii) There are **NINE** questions in this paper.
- (iii) Attempt **FIVE** questions in all.
- (iv) Question No. 1 is compulsory.

1. Choose the correct option/Answer the following (any seven) : 2×7=14

- (a) If the op-amp (in Fig. 1) is ideal, the output voltage  $V_{out}$  will be equal to

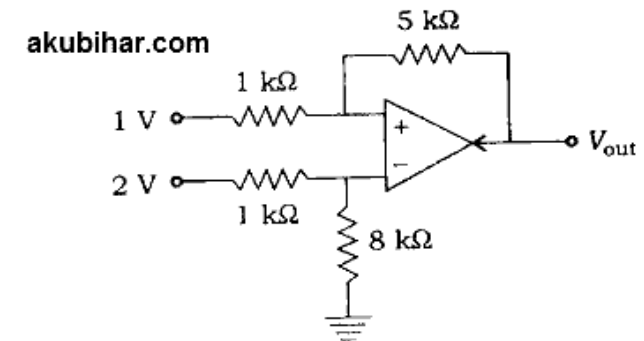


Fig. 1

- (i) 5.6 V
- (ii) 6 V
- (iii) 14 V
- (iv) 17 V

( 2 )

akubihar.com

- (b) In Fig. 2, capacitor is initially uncharged. At  $t=0$ , switch  $S$  is closed. The voltage  $V_C$  across capacitor at  $t=2 \text{ msec}$  is

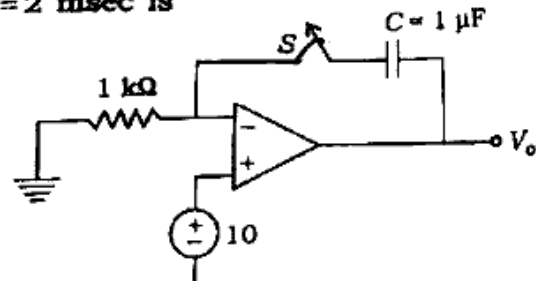


Fig. 2

- (i) 0 V                      (ii) 6.3 V  
(iii) 9.45 V                (iv) 20 V

akubihar.com

- (c) In Fig. 3, the  $V-I$  characteristics of the diode is described by  $I = I_0 (e^{V/V_T} - 1)$   
 $V_T = 25 \text{ mV}$ ,  $I_0 = 1 \mu\text{A}$ ,  $V$  is the voltage across the diode. For an input voltage of  $-1 \text{ V}$ , the output voltage is

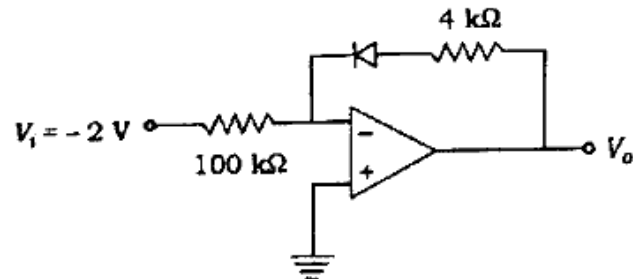


Fig. 3

- (i) 0 V                      (ii) 0.156 V  
(iii) 0.7 V                (iv) 1.1 V

AK16/661

( Continued )

( 3 )

- (d) In Fig. 4,  $R_c = R_a = R_b = R_d = 200 \Omega$ . Then o/p voltage is

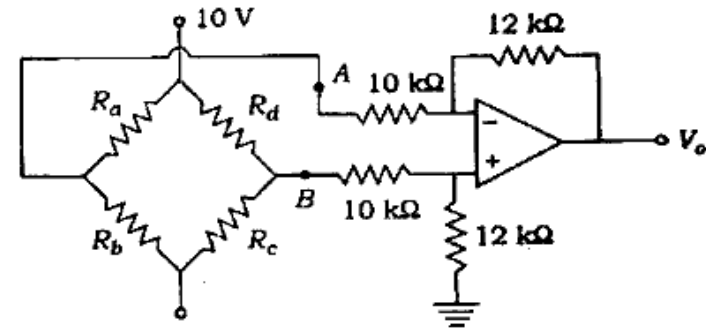


Fig. 4

- (i) 0 V                      (ii) 10 V  
(iii) 100 V                (iv) 120 V

akubihar.com

- (e) A 10-bit A/D converter is used to digitize an analog signal in the range  $0 \text{ V}$  to  $10 \text{ V}$ . The maximum peak-to-peak ripple voltage that can be allowed in the d.c. supply voltage is nearly

- (i) 100 mV  
(ii) 10 mV  
(iii) 25 mV  
(iv) 5 mV

akubihar.com

AK16/661

( Turn Over )

( 4 )

akubihar.com

- (f) If the resolution of D/A converter is approximately 5% of its full-scale range, then it is an/a
- (i) 8-bit converter
  - (ii) 10-bit converter
  - (iii) 12-bit converter
  - (iv) 16-bit converter
- (g) The open-loop gain of an op-amp falls to zero decibel at 10 MHz. What is its unity gain crossover frequency?
- (i) 1 MHz
  - (ii) 10 MHz
  - (iii) 5 MHz
  - (iv) Indeterminate from given data
  - (v) None of the above

- (h) Fig. 5 shows an op-amp voltage-follower circuit. This circuit is being driven by another circuit with output resistance of 100 k $\Omega$ . What should be the value of R?

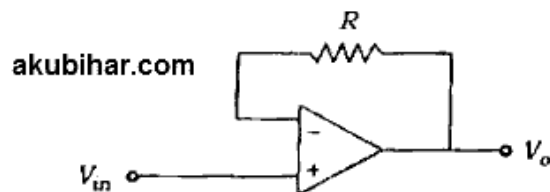


Fig. 5

- (i) 100 k $\Omega$
- (ii) 0
- (iii) 10 k $\Omega$
- (iv) 1 M $\Omega$
- (v) None of the above

( 5 )

akubihar.com

- (i) Capture range of a phase-locked loop is
- (i) equal to its lock range
  - (ii) less or equal to lock range
  - (iii) always greater than lock range
  - (iv) greater or equal to lock range
  - (v) None of the above
- (j) Define narrow band-pass filter.
2. (a) Discuss the criteria for selecting a transducer.
- (b) Discuss the ideal op-amp's electrical characteristics. 7+7
3. (a) Draw the circuit diagram of practical integrator and derive the input-output relations for the same.
- (b) Discuss one application where instrumentation amplifier is used. 7+7
- akubihar.com
4. (a) Discuss different features of instrumentation amplifier.
- (b) Design a low-pass filter having a cut-off frequency of 2 kHz with a pass-band gain of 2. 7+7

( 6 )

akubihar.com

5. (a) For a 5-bit ladder type D/A converter, if the input levels are  $0 = 0\text{ V}$  and  $1 = +10\text{ V}$ , what are the output voltages for each bit?
- (b) Discuss one method of D/A conversion with circuit diagram. 7+7
6. (a) Discuss about different pressure sensitive primary devices (transducers).
- (b) Draw the block diagram and operating principles of phase-locked loop. 7+7
7. (a) Determine the free-running frequency  $f_{out}$ , the lock range  $f_L$ , and the capture range  $f_C$  of Fig. 6 :

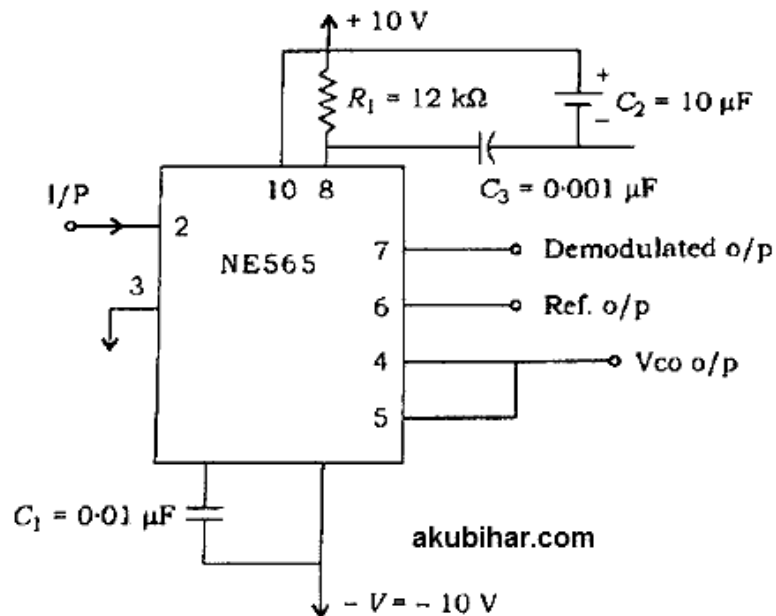


Fig. 6

( 7 )

- (b) How can voltage to current converter be used for diode match finder? 7+7  
akubihar.com
8. (a) Draw the circuit and discuss the working principles of Schmitt trigger.
- (b) Using  $R_1 = 100\ \Omega$ ,  $R_L = 56\ \text{k}\Omega$ ,  $V_{in} = 1\ \text{VPP}$  sine wave and op-amp with supply voltage ( $\pm 15\ \text{V}$ ). Construct a Schmitt trigger circuit. Determine the threshold voltage  $V_{ut}$  and  $V_{lt}$  and draw the output waveform. 7+7
9. (a) Draw the block diagram of intelligent instrument and discuss its different blocks.
- (b) Draw the op-amp based sample and hold circuit. Explain its operation. 7+7

\*\*\*

akubihar.com