

## B.Tech 5th Semester Exam., 2021

( New Course )

LINEAR INTEGRATED CIRCUITS  
AND APPLICATIONS

Time : 3 hours

Full Marks : 70

Instructions :

- (i) The marks are indicated in the right-hand margin.
- (ii) There are **EIGHT** questions in this paper.
- (iii) Attempt **FIVE** questions in all.
- (iv) Question No. 1 is compulsory.

1. Answer any seven of the following questions :

2×7=14

- (a) What is a comparator?
- (b) Define settling time of D/A converter.
- (c) How does a precision rectifier differ from the conventional rectifier?
- (d) What output voltage would be produced by a D/A converter whose output range is 0 to 10V and whose input binary number is 0101 for a 4-bit DAC?

- (e) What is the main drawback of dual slope ADC?
- (f) Give the classification of voltage regulators with example.
- (g) A PLL frequency multiplier has an input frequency of  $f$  and a decade counter is included in the loop. What will be the frequency of the PLL output?
- (h) Why is frequency compensation required in operational amplifiers?
- (i) Draw a sample and hold circuit.
- (j) Which is fastest ADC? Give proper reasoning.

2. (a) With the help of neat circuit diagram, explain the working of a basic bandgap voltage reference. 7

(b) Explain the steps used for fabrication of integrated diodes with necessary diagrams. 7

3. (a) Sketch the basic circuit using OPAMP to perform the mathematical operation of differentiation and explain its working. What are the limitations of the basic differentiator? 7

(b) Define output offset voltage. Explain the methods to nullify offset voltage. 7

4. (a) Explain the working of multiplier using suitable OPAMP circuit diagram and supporting equations. 7
- (b) Draw the circuit diagram of a phase locked loop (PLL) used as amplitude modulation (AM) detector and explain its operation. 7
5. (a) Draw the block diagram and explain principle of working, characteristic and applications of a frequency synthesizer. 7
- (b) Explain the working of a switched capacitor filter with supporting circuit diagram. How can a resistor be realized using switched capacitor? 7
6. (a) Explain the working of weighted resistor D/A converter with circuit diagram. 7
- (b) With a suitable diagram, explain the working of successive approximation type A/D converter. 7
7. (a) Discuss the principle of operation of NES65 PLL circuit. 7
- (b) If an IC 555 timer is used to generate a ramp voltage with constant collector current of 1 mA,  $V_{CC} = 15V$  and  $C = 0.1 \mu F$ , what would be the slope of the ramp generated? How much is the peak value of the ramp generated? What is the duration of the ramp? 7

8. (a) Design a timer which should turn on heater immediately after pressing a push button and should hold heater in ON state for 6 seconds. 7
- (b) Explain the monostable operation of 555 timer. 7

\*\*\*

<https://www.akubihar.com>

Whatsapp @ 9300930012

Send your old paper & get 10/-

अपने पुराने पेपर्स भेजे और 10 रुपये पायें,

Paytm or Google Pay से