

2012

BASIC ELECTRICAL ENGINEERING

Time : 3 hours akubihar.com Full Marks : 70

Instructions :

- (i) The figures in the margin indicate full marks.
- (ii) There are **NINE** questions in this paper.
- (iii) Attempt **FIVE** questions in all.
- (iv) Question No. 1 is compulsory.

1. Choose the correct answer (any seven) :

2×7=14

- (a) An electric current is the
 - (i) random movement of electrons in a conductor
 - (ii) movement of free electrons predominately in one direction
 - (iii) pressure difference between two poles
 - (iv) power that causes drift of electrons

- (b) Correct form of Ohm's law is
 - (i) $I = VR$
 - (ii) $V \propto I$
 - (iii) $V = IR$
 - (iv) Both (i) and (iii)
- (c) Resistance of a wire always increases, if
 - (i) temperature is reduced
 - (ii) temperature is increased
 - (iii) number of free electrons available become less
 - (iv) number of free electrons available become more akubihar.com
- (d) A 200 W, 230 V lamp is connected across 115 V supply. The lamp will draw power
 - (i) slightly more than 50 W
 - (ii) slightly less than 50 W
 - (iii) exactly 100 W
 - (iv) exactly 50 W
- (e) Superposition theorem is not applicable for
 - (i) voltage calculations
 - (ii) bilateral elements
 - (iii) power calculations
 - (iv) passive elements

- (f) Maxwell's loop current method of solving electrical networks
- (i) uses branch currents
 - (ii) utilizes Kirchhoff's voltage law
 - (iii) is confirmed to single-loop circuits
 - (iv) is a network reduction method
- (g) While Thevenizing a circuit between two terminals, V_{TH} is equal to
- (i) short-circuit terminal voltage
 - (ii) open-circuit terminal voltage
 - (iii) net voltage available in the circuit
 - (iv) e.m.f. of the battery nearest to the terminals
- (h) The unit of flux density is
- (i) tesla
 - (ii) A/mm^2
 - (iii) N/m^2
 - (iv) Wb/m
- (i) The magnetic field required to reduce the residual magnetization to zero is called
- (i) retentivity
 - (ii) coercivity
 - (iii) hysteresis
 - (iv) saturation magnetization

- (j) The r.m.s. value of a sine wave is 100 A. Its peak value is

- (i) 70.7 A
- (ii) 141 A
- (iii) 150 A
- (iv) 282.8 A

2. (a) Use the node voltage method to determine voltage V in the circuit shown in Fig. 1. Also find the current delivered by the controlled source.

7

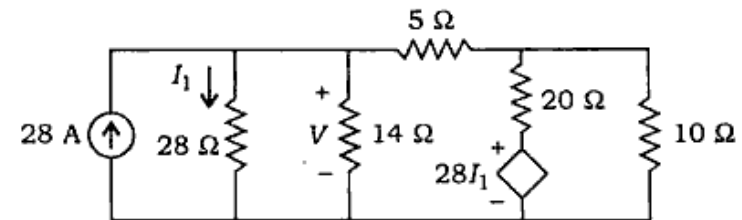


Fig. 1

- (b) Use the loop current method to find the current I in the circuit shown in Fig. 2.

7

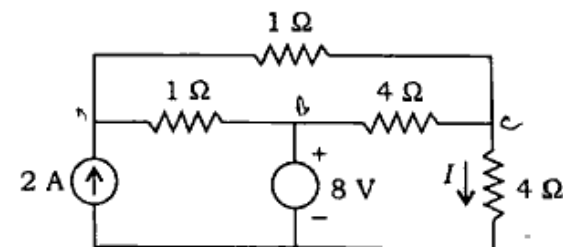


Fig. 2

(5)

akubihar.com

3. (a) Use superposition theorem to find the current in different branches of the circuit shown in Fig. 3.

7

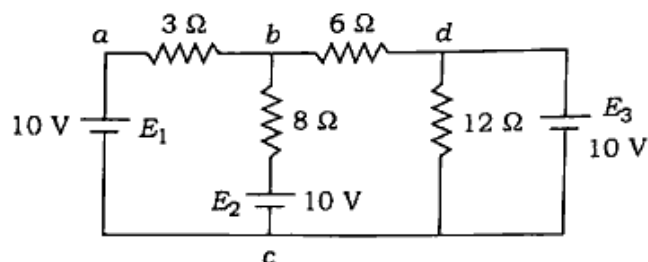


Fig. 3

- (b) Use Thevenin's theorem to find the current through the $40\ \Omega$ resistance in the circuit shown in Fig. 4.

7

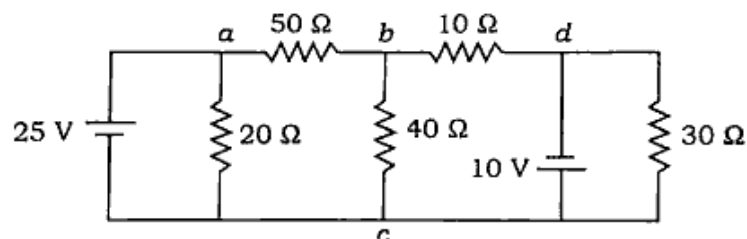


Fig. 4

4. (a) Define the following :

8

- (i) Form factor
- (ii) Peak factor
- (iii) Power factor
- (iv) Resonance

(6)

- (b) Determine the r.m.s. and average values of the waveform shown in Fig. 5.

6

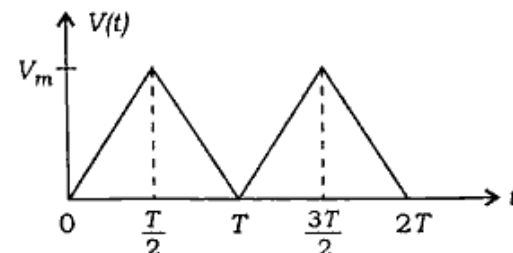


Fig. 5

5. (a) State and explain maximum power theorem.

6

- (b) Use maximum power transfer theorem to determine R so that maximum power is transferred to it (see Fig. 6). Determine the value of this power.

8

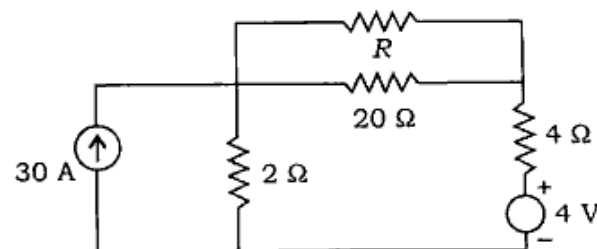


Fig. 6

6. (a) A balanced delta-connected load of impedance $(16 + j12)\ \Omega$ per phase is connected to a 3-phase, 400 V supply. Determine the phase current, line current, power factor, power, reactive power and total VA. Also draw the phase diagram.

7

- (b) Explain the following : 7
- (i) Balanced and unbalanced systems
- (ii) Phase sequence
7. (a) Define apparent, active and reactive power. Derive their formulas. Discuss their significance in a.c. systems. 7
- (b) A coil has a resistance to reactance ratio of 170 at 10^6 Hz. Its inductance is 250 μ H. A variable capacitor is connected in parallel with the coil. Find the value of C so that resonant frequency is 10^6 Hz. Also find impedance at resonance. 7
8. (a) An iron ring has a mean circumference of 75 cm and a cross-sectional area of 5 cm². Its magnetizing coil has 140 turns. Use the following data to find the exciting current for a flux of 6.3×10^{-4} Wb. Also find μ_r : 8
- | | | | | |
|-----------|-----|-----|-----|-----|
| B (tesla) | 0.9 | 1.1 | 1.2 | 1.3 |
| H (A/m) | 260 | 450 | 600 | 820 |
- (b) Define reluctance and explain its significance. Which has higher reluctance—an air gap or an iron path? Why? Prove that $B = \mu H$. 6
9. (a) How can the insulation resistance of a cable be measured? Explain the method used. 7
- (b) It is desired to convert a moving-coil meter having a full-scale deflection of 2 mA and resistance 20 Ω into a voltmeter of 100 V range. Find the value of series resistance. 7

akubihar.com