

Code : 041401

(2)

B.Tech 4th Semester Exam., 2018

BASIC ELECTRONICS

Time : 3 hours

Full Marks : 70

Instructions :

- (i) The marks are indicated in the right-hand margin.
- (ii) There are **NINE** questions in this paper.
- (iii) Attempt **FIVE** questions in all.
- (iv) Question No. 1 is compulsory.

1. Choose the correct answer of the following
(any seven) : 2×7=14

- (a) When checking a diode, low resistance readings both ways indicate the diode is
- (i) open
 - (ii) satisfactory
 - ~~(iii) faulty~~
 - (iv) not the problem

8AK/343

(Turn Over)

- (b) Which of the following is the correct relationship between I_B and I_E ?

(i) $I_B = \beta I_E$

(ii) $I_B = I_E$

~~(iii) $I_B = (\beta + 1) I_E$~~

~~(iv) $I_E = (\beta + 1) I_B$~~

- (c) If a 169.7 V half-wave peak has an average voltage of 54 V, what is the average of two full-wave peaks?

(i) 119.9 V

(ii) 108.0 V

~~(iii) 115.7 V~~

(iv) 339.4 V

- (d) The Q-point on a load line may be used to determine

(i) V_C

(ii) V_{CC}

(iii) V_B

(iv) I_C

8AK/343

(Continued)

(3)

(e) For the BJT to operate in the active (linear) region, the base-emitter junction must be _____-biased and the base-collector junction must be _____-biased.

- (i) forward, forward
- ~~(ii)~~ forward, reverse
- (iii) reverse, reverse
- (iv) reverse, forward

(f) What is the level of drain current I_D for gate-to-source voltages V_{GS} less than (more negative than) the pinch-off level?

- ~~(i)~~ Zero ampere
- ~~(ii)~~ I_{DSS}
- (iii) Negative value
- (iv) Undefined

(g) How much times reverse saturation current will increase, if temperature increases 15°C ?

- (i) 2.52
- (ii) 4.62
- (iii) 4.12
- (iv) 2.82

(4)

(h) The total discharge time for the capacitor in a clamper having $C = 0.01 \mu\text{F}$ and $R = 500 \text{ k}\Omega$ is

- ~~(i)~~ 5 ms
- (ii) 25 ms
- (iii) 2.5 ms
- (iv) 50 ms

(i) How many op-amps are required to implement the equation $V_0 = V_1$?

- (i) 2
- (ii) 3
- (iii) 4
- (iv) 1

(j) A non-inverting closed-loop op-amp circuit generally has a gain factor

- (i) less than one
- ~~(ii)~~ greater than one
- (iii) of zero
- (iv) equal to one

2. (a) Differentiate between an ideal and a practical voltage source. Give their graphical representations and convert 10 V voltage source with its series resistance of 2Ω into its equivalent current source.

(5)

(b) Explain the working of a shunt capacitor filter and derive an approximate expression for ripple factor in half-wave rectifier with shunt capacitor filter. 7+7=14

3. (a) Compare the differences between JFET and MOSFET and also prove that the transconductance g_m of a JFET is given by

$$g_m = \frac{2}{|V_P|} \sqrt{I_{DS} I_{DSS}}$$

(b) Explain the UJT as a relaxation oscillator. 9+5=14

4. (a) Explain Zener and avalanche breakdown in semiconductors.

(b) Define α and β of a transistor. Also derive the relationship between them. 8+6=14

5. (a) Sketch the output characteristics for N-channel JFET with gate-source shorted (i.e., $V_{GS} = 0$). How are ohmic, pinch off and breakdown regions created?

(b) Explain the basic structure and working of a P-channel JFET. 8+6=14

6. (a) Compare the characteristics of CB, CE and CC configurations of a transistor. Draw the circuit of a common-collector

8AK/348

(Turn Over)

(6)

transistor configuration and explain its operation. Also derive the relation between γ and α current amplification factors.

- (b) A collector to base circuit has $V_{CB} = 24$ V, $R_B = 180$ k Ω , $R_C = 3.3$ k Ω and $V_{CE} = 10$ V. Calculate h_{FE} and determine V_{CE} when a new transistor is replaced having $h_{FE} = 120$. 8+6=14

7. (a) An inverting op-amp has $R_f = 100$ k Ω and $R_1 = 2$ k Ω . Find the voltage gain of the amplifier. Also find the amplifier input resistance, input current and the output voltage if the input voltage is 0.1 V. Assume op-amp to be ideal.

(b) Explain the working of an op-amp as an integrator circuit. 8+6=14

8. (a) Explain a voltage-shunt feedback amplifier with suitable example.

(b) In a transistor circuit, load resistance is 5 k Ω and quiescent current is 1.2 mA. Determine the operating point when the battery voltage $V_{CC} = 12$ V. How will the Q-point change when the load resistance is changed from 5 k Ω to 7.5 k Ω ? 6+8=14

8AK/348

(Continued)

(7)

9. (a) Describe the structure, symbol and operation of SCR with the help of suitable diagrams.
- (b) In an N-type semiconductor, the Fermi level lies 0.3 eV below the conduction band at 27 °C. If the temperature is increased to 55 °C, find the new position of the Fermi level. $7+7=14$

AKUbihar.com

AKUbihar.com

AKUbihar.com

AKUbihar.com