

B.Tech 4th Semester Exam., 2019

BASIC ELECTRONICS

Time : 3 hours

Full Marks : 70

Instructions :

- (i) The marks are indicated in the right-hand margin.
- (ii) There are **NINE** questions in this paper.
- (iii) Attempt **FIVE** questions in all.
- (iv) Question No. 1 is compulsory.

1. Answer the following questions briefly (any seven) : 2×7=14

- (a) If doping level in a crystal diode is increased, what will happen to the width of depletion layer?
- (b) How does Zener diode behave in the breakdown region?

(c) At which voltage avalanche occurs in a diode?

(d) If the maximum DC current rating of diodes in bridge rectifier is 2A, then what is the maximum DC load current?

(e) A half-wave rectifier has an input voltage of 240 V r.m.s. If the step-down transformer has a turns ratio of 8 : 1, what is the peak load voltage? Ignore diode drop.

(f) If $V_{CC} = +20$ V, voltage-divider resistor R_1 is $5k\ \Omega$ and R_2 is $2k\ \Omega$, what is the base bias voltage?

(g) When does thermal runaway occur?

(h) With the E-MOSFET, what is the value of drain current when gate input voltage is zero?

- (i) What is the bandwidth of an ideal operational amplifier?
- (j) If gate current is increased, then what will happen to anode-cathode voltage at which SCR closes?

2. (a) Differentiate between ideal and practical voltage sources. Give their graphical representations and convert 20 V voltage source with its series resistance of $10\ \Omega$ into its equivalent current source.

(b) Derive continuity equation for carrier concentration in body of a semiconductor. 7+7=14

3. (a) Derive the expressions for (i) I_{rms} , (ii) I_{dc} , (iii) ripple factor and (iv) efficiency of rectification; in case of full-wave rectifier.

- (b) Draw a sketch to show various currents in an $N-P-N$ transistor and derive the relationship between various components. 6+8=14

4. (a) A 4 : 1 transformer supplies a bridge rectifier that is driving a load of 400 ohms. If the transformer input is 230 V/50 Hz supply, calculate the d.c. output voltage, $P-I-V$ and the output frequency. Assume the rectifier diodes to be ideal. <http://www.akubihar.com>

(b) Draw diode $I-V$ characteristics, discuss its temperature dependence and obtain the expression for diode dynamic resistance. 7+7=14

5. (a) Using a common collector $N-P-N$ transistor configuration, derive the expressions for voltage gain and current gain.

(5)


- (b) Design the voltage divider bias circuit to operate from 20 V supply. The bias conditions are $V_{CE} = 5$ V, $V_E = 7$ V and $I_C = 5$ mA. 7+7=14

6. (a) A collector to base circuit has $V_{CB} = 30$ V, $R_B = 200$ k Ω , $R_C = 4$ k Ω and $V_{CE} = 20$ V. Calculate h_{FE} and determine V_{CE} , when a new transistor is replaced having $h_{FE} = 150$.
- (b) Draw two-dimensional structure of n-channel MOSFET. Explain its working. 7+7=14

7. (a) An n-channel FET is utilized by amplifier shown in figure for which $V_P = -3.0$ V and $I_{DSS} = 2$ mA. It is desired to bias the circuit at $I_D = 1$ mA,

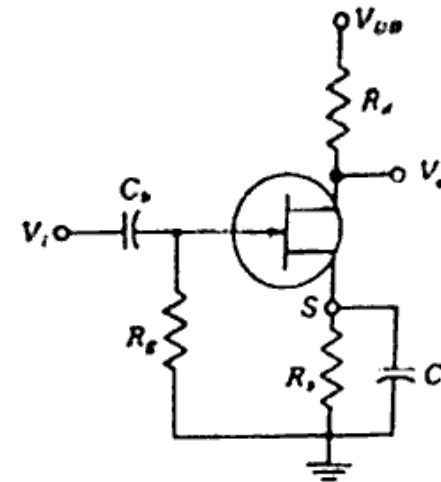(6)

using $V_{DD} = 26$ V. Assume $r_d \gg R_d$.
Find (i) V_{GS} , (ii) g_m and (iii) R_S .



- (b) Explain the working of BJT voltage-divider bias circuit. Derive the expression for Q-point (I_{CQ} , V_{CEQ}) in terms of circuit parameters. 7+7=14

8. (a) Explain a voltage-series feedback amplifier with suitable example.
- (b) Using an op-amp, explain the circuits for a voltage gain amplifier (with least components) and current to voltage converter. 7+7=14

(Continued)

9. (a) Explain the working principle of unijunction transistor (UJT).

(b) Describe the structure, symbol and operation of SCR with the help of suitable diagrams. 7+7=14

<http://www.akubihar.com>

Whatsapp @ 9300930012

Your old paper & get 10/-

पुराने पेपर्स भेजे और 10 रुपये पायें,

Paytm or Google Pay से