

Code : 041402

akubihar.com

B.Tech. 4th Semester Exam., 2014**DIGITAL ELECTRONICS**

Time : 3 hours

Full Marks : 70

Instructions :

- (i) The marks are indicated in the right-hand margin.
- (ii) There are **NINE** questions in this paper.
- (iii) Attempt **FIVE** questions in all.
- (iv) Question No. 1 is compulsory.

1. Choose the correct option from the following
(any seven) : 2×7=14

(a) A quantity having continuous wave is

- (i) a digital quantity
- (ii) an analog quantity
- (iii) a binary quantity
- (iv) a natural quantity

(b) The sum of $11010 + 01111$ equals

- (i) 101001
- (ii) 101010
- (iii) 110101
- (iv) 101000

akubihar.com

- (c) The output of a gate is low if and only if its input are HIGH. It is true for

- (i) AND
- (ii) XNOR
- (iii) NOR
- (iv) NAND

- (d) An example of a standard SOP expression is

- (i) $\overline{A}\overline{B} + \overline{A}BC + A\overline{B}\overline{D}$
- (ii) $\overline{A}BC + ACD$
- (iii) $\overline{A}\overline{B} + \overline{A}B + AB$
- (iv) $AB\overline{C}D + \overline{A}B + \overline{A}$

- (e) To implement the expression of $\overline{A}BCD + \overline{A}\overline{B}CD + AB\overline{C}D$, it takes one OR gate and

- (i) one AND gate
- (ii) three AND gates
- (iii) three AND gates and four inverters
- (iv) three AND gates and three inverters

- (f) The invalid state of an S-R latch occurs when

- (i) $S = 1, R = 0$
- (ii) $S = 0, R = 1$
- (iii) $S = 1, R = 1$
- (iv) $S = 0, R = 0$

(g) The device used to convert a binary number to a 7-segment display format is

(i) multiplexer

(ii) encoder

(iii) decoder

(iv) register

(h) An asynchronous counter differs from a synchronous counter in

(i) the number of states in its sequence

(ii) the method of clocking

(iii) the type of flip-flop used

(iv) the value of the modulus

(i) A stage in a shift register consists of

(i) a latch

(ii) a flip-flop

(iii) a byte of storage

(iv) four bits of storage

(j) A 32-bit data word consists of

(i) 2 bytes

(ii) 4 nibbles

(iii) 4 bytes

(iv) 3 bits and 1 nibble

2. (a) Make a K-map for the function

$$F = A\bar{B} + AC + A\bar{D} + AB + ABC \quad 5$$

(b) Express F , in standard SOP and POS form. 5

(c) Minimize F and realize the minimal expression using NOR gate only. 4

3. (a) Prove the following algebraically :

$$2^{1/2} + 2^{1/2} = 5$$

$$(i) (A+B)(A+\bar{B}) = A \oplus B$$

$$(ii) (A+B)(A+\bar{B})(\bar{A}+B) = AB$$

(b) Convert decimal number 75 into Grey code. 4

(c) Verify a two-level AND-OR gate is equivalent to NAND-NAND. 5

4. (a) Draw a circuit diagram of an RTLEX-OR gate. Explain its operation. 7

(b) Draw a circuit diagram of DTL gate and explain it. What are fan-in and fan-out? How will you increase the fan-out of the gate? 7

(5)

5. (a) Design a full adder using only NAND gate. 7

(b) Design a 8 to 1 line multiplexer using 4 to 1 line multiplexer. 7

6. (a) Differentiate between synchronous and asynchronous counter. 7

(b) Design a 4-bit synchronous up counter. 7

7. (a) Explain the following flip-flops with their diagrams and truth tables : 7

(i) SR F/F

(ii) J-K F/F

(iii) D F/F

(iv) T F/F

$$\frac{8}{4} = 2$$

(b) Design D F/F from J-K F/F. 7

8. (a) Explain the working principle of a successive approximation ADC with the help of circuit diagram. 7

(b) Find the output voltage from a 5-bit ladder D/A converter which has a digital input of 11010. Assume 0 = 0 V and 1 = +10 V. 7

(6)

akubihar.com

9. Write short notes on any two of the following : 7×2=14

(a) Data transfer in a shift register

(b) ROM

(c) Astable multivibrator using 555

(d) Digital comparator

akubihar.com